

**Code No: 126ZH****JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B. Tech III Year II Semester Examinations, December - 2018****ELECTRICAL AND ELECTRONICS INSTRUMENTATION****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART - A****(25 Marks)**

- 1.a) Why the scale of Moving Iron instrument is calibrated non- linearly? [2]
- b) What is the extension procedure of electrostatic voltmeter? [3]
- c) How the D.C. potentiometer is standardized? [2]
- d) Draw the equivalent circuit and phasor diagram of a current transformer. [3]
- e) What is Tri-vector Meter? [2]
- f) What is creeping in an energy meter and how it can be minimised? [3]
- g) Mention the purpose of Desauty bridge and Schering bridge ? [2]
- h) Derive an expression for deflection current ( $I_g$ ) of an unbalanced Wheatstone's bridge. [3]
- i) How Delayed time base system can be operated in Oscilloscope. [2]
- j) What are active and passive transducers? Give examples. [3]

**PART - B****(50 Marks)**

- 2.a) With a neat diagram explain in detail the construction of PMMC instrument.
- b) A moving coil instrument gives a full scale deflection of 10mA when the potential difference across its terminals is 150mV. Calculate
  - i) The shunt resistance for a full scale deflection corresponding to 100A and 130A.
  - ii) The series resistance for full scale reading with 600V. Calculate the power dissipated in each case. [5+5]

**OR**

- 3.a) State the basic requirement of any measuring instruments. How the various measuring instruments are classified?
- b) Explain the working principle of moving iron instrument and write advantages. [5+5]
- 4.a) Explain how wattmeter is calibrated using D.C potentiometer
- b) What is volt-ratio box? Design a volt ratio box with a resistance of 50 $\Omega$ /Volt, and ranges 25V, 50V, 75V, 150V and 300V. The volt-ratio box is to be used with a potentiometer having a measuring range of 1.6V. [5+5]

**OR**

- 5.a) Explain the construction and working principle of a polar type potentiometer with a neat sketch.
- b) Why a potentiometer does not load the voltage source whose voltage is being determined. [6+4]

- 6.a) Explain the special features incorporated in an electro-dynamometer type of wattmeter so that it can be used for low power factor applications.  
b) Discuss in detail about maximum demand meters. [5+5]

**OR**

- 7.a) Derive the torque equation for induction type single phase energy meter.  
b) A 50 A, 230 V, 1-phase energy meter on full load test makes 61 revolutions in 37 secs. If the normal disc speed is 520 revolutions per kwh, find the percentage error? [5+5]
- 8.a) Why Kelvin's bridge is preferred? Derive the bridge balance equation for the Kelvin's Bridge?  
b) Explain the construction and working principle of megger to measure high resistances. [5+5]

**OR**

- 9.a) Draw the Maxwell's bridge circuit and derive the expression for the unknown element at balance.  
b) An A.C bridge has the following elements: Arm AB:  $R_1 = 600\Omega$ ,  $G = 0.4\mu F$ . Arm BC:  $R_2 = 400\Omega$ ,  $C_2 = 2\mu F$ . Elements in arm AB are in parallel. Elements in arm BC are in series. Arm CD:  $R_3 = 1.4K\Omega$ . Arm AD has unknown resistance  $R_x$  with usual notation. Find the value of  $R_x$  and the frequency at which the bridge is in balance. [5+5]

- 10.a) What is the use of LVDT? Discuss its basic principle of operation.  
b) Explain the principle of Strain gauges and give their constructional details. [5+5]

**OR**

- 11.a) With a neat diagram, explain the working of CRT.  
b) Write short notes on Photo Diodes. [5+5]

---ooOoo---